

BSSE Applied Physics

Quiz 2

Question:

10 Marks

Solve the following circuit to find the unknown currents I_1 , I_2 and I_3

